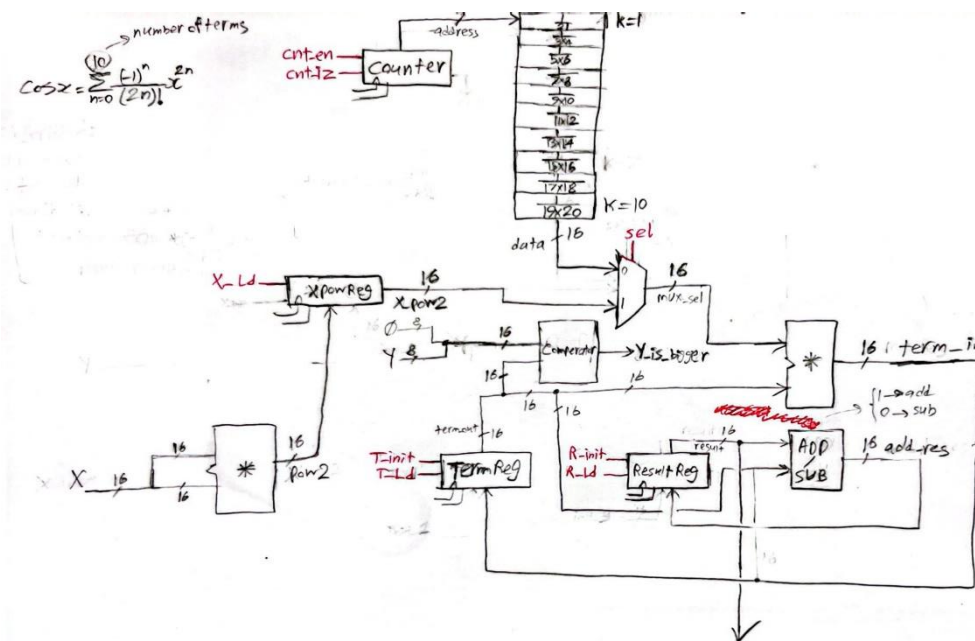


## CA6 Report

Design Phase:

Part 1 and 3:

Datapath design:



## Part 2:


Algorithm

```

result = 1
term = 1
for (k = 1; k <= n; k++) {
    term = term * (x^2)
    term = term * 1 / (k * (k + 1))
    result = result + (-1)^k * term
}
    
```

$\min Y = 2 \times 10^{-8}$   
 $\frac{\pi^n}{n!}$

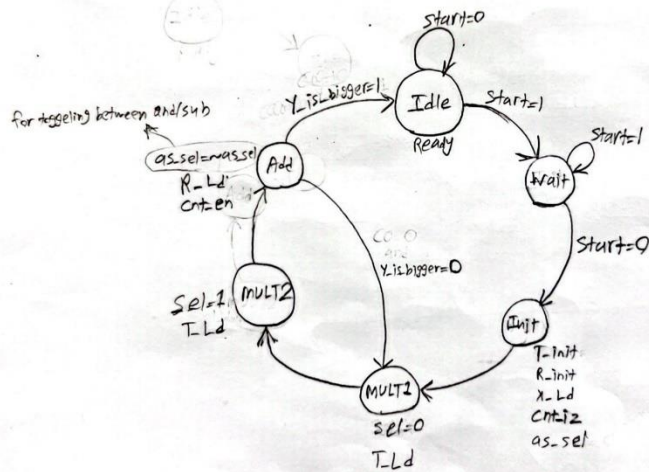precision  $\frac{\pi^n}{n!} > 2 \times 10^{-8} \rightarrow n = 20$   
 $\rightarrow 10 \text{ terms}$



CS Scanned with CamScanner


## Part 4:

```


1 module controller (input clk,rst,y_bigger,start, output reg cnt_en,cnt_iz,x_ld,t_ld,t_init,sel,r_ld,r_init,as_sel,ready);
2     reg[2:0] ns,ps;
3     parameter [2:0] Idle = 0, Wait = 1, Init = 2, Mult1 = 3, Mult2 = 4, Add = 5;
4     always @(ps,y_bigger) begin
5         {cnt_en,cnt_iz,x_ld,t_ld,t_init,sel,r_ld,r_init,as_sel,ready} = 10'b0;
6         case(ps)
7             Idle : begin ns = start ? Wait : Idle; ready = 1'b1; end
8             Wait : begin ns = start ? Wait : Init; end
9             Init : begin ns = Mult1; t_init = 1'b1; r_init = 1'b1; x_ld = 1'b1; cnt_iz = 1'b1; end
10            Mult1 : begin ns = Mult2; sel = 1'b0; t_ld = 1'b1; end
11            Mult2 : begin ns = Add; sel = 1'b1; t_ld = 1'b1; end
12            Add : begin ns = y_bigger ? Idle : Mult1; r_ld = 1'b1; cnt_en = 1'b1; end
13        endcase
14    end
15    always @(posedge clk,posedge rst) begin
16        if(rst)
17            ps <= Idle;
18        else
19            ps <= ns;
20        end
21 endmodule

```

 From line 4 to 14, we have the combinational part of the controller and from line 15 to 20, we have the sequential part of the controller. Here is the Hoffman model of the controller:



## Part 5:

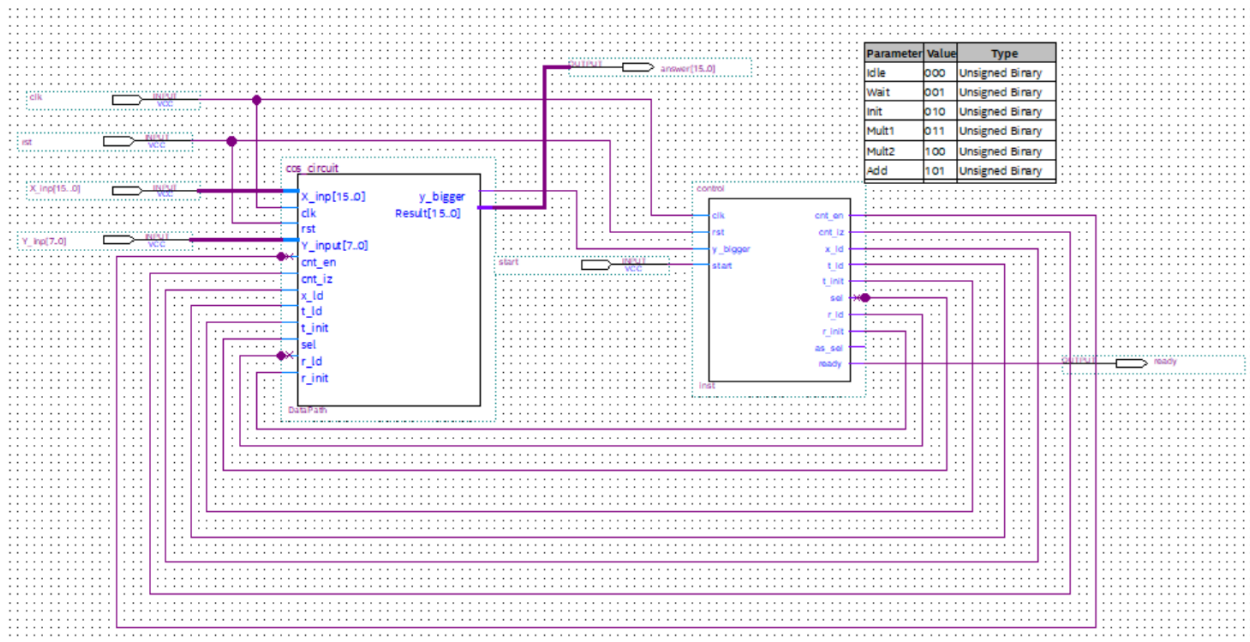

## Implementation Phase:


## Controller part:

### Code:


```
1 module controller (input clk,rst,y_bigger,start, output reg cnt_en,cnt_iz,x_ld,t_ld,t_init,sel,r_ld,r_init,as_sel,ready);
2     reg[2:0] ns,ps;
3     parameter [2:0] Idle = 0, Wait = 1, Init = 2, Mult1 = 3, Mult2 = 4, Add = 5;
4     always @(ps,y_bigger) begin
5         {cnt_en,cnt_iz,x_ld,t_ld,t_init,sel,r_ld,r_init,as_sel,ready} = 10'b0;
6         case(ps)
7             Idle : begin ns = start ? Wait : Idle; ready = 1'b1; end
8             Wait : begin ns = start ? Wait : Init; end
9             Init : begin ns = Mult1; t_init = 1'b1; r_init = 1'b1; x_ld = 1'b1; cnt_iz = 1'b1; end
10            Mult1 : begin ns = Mult2; sel = 1'b0; t_ld = 1'b1; end
11            Mult2 : begin ns = Add; sel = 1'b1; t_ld = 1'b1; end
12            Add : begin ns = y_bigger ? Idle : Mult1; r_ld = 1'b1; cnt_en = 1'b1; end
13        endcase
14    end
15    always @(posedge clk,posedge rst) begin
16        if(rst)
17            ps <= Idle;
18        else
19            ps <= ns;
20        end
21    endmodule
```

### Number of used elements for building the circuit:

Flow Status	Successful - Mon Jan 08 18:39:13 2024
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	control
Top-level Entity Name	control
Family	Cyclone IV GX
Device	EP4CGX15BF14A7
Timing Models	Final
Total logic elements	7 / 14,400 ( < 1 % )
Total registers	6
Total pins	14 / 81 ( 17 % )
Total virtual pins	0
Total memory bits	0 / 552,960 ( 0 % )
Embedded Multiplier 9-bit elements	0
Total GXB Receiver Channel PCS	0 / 2 ( 0 % )
Total GXB Receiver Channel PMA	0 / 2 ( 0 % )
Total GXB Transmitter Channel PCS	0 / 2 ( 0 % )
Total GXB Transmitter Channel PMA	0 / 2 ( 0 % )
Total PLLs	0 / 3 ( 0 % )

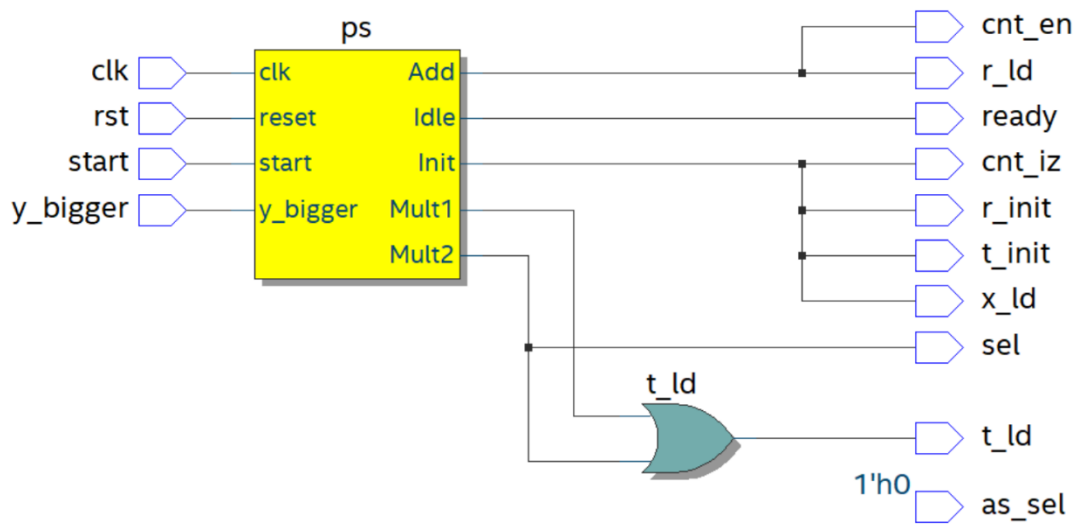


## Controller Testbench:

 




When y becomes bigger than term, we will be back to the Idle state and Ready will be 1.

## Datapath part:

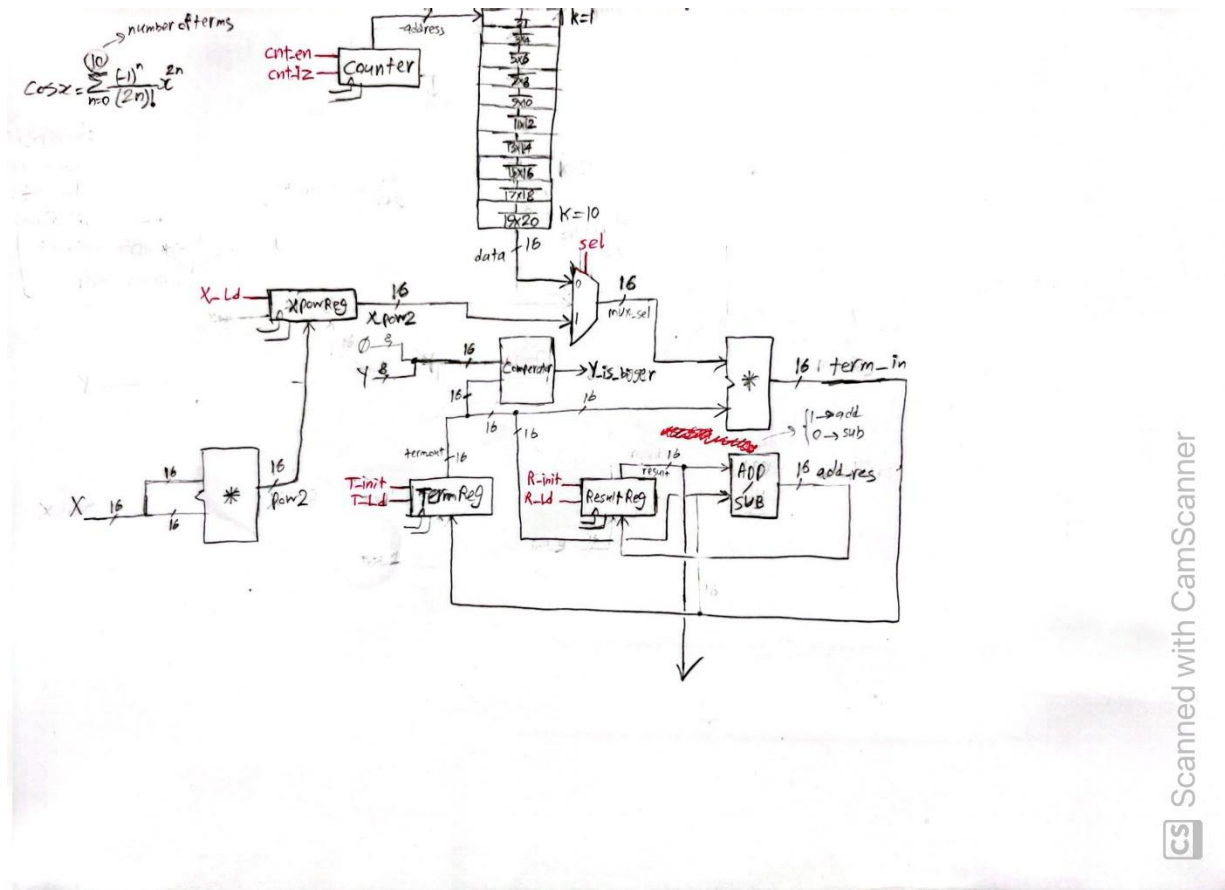

Block diagram:

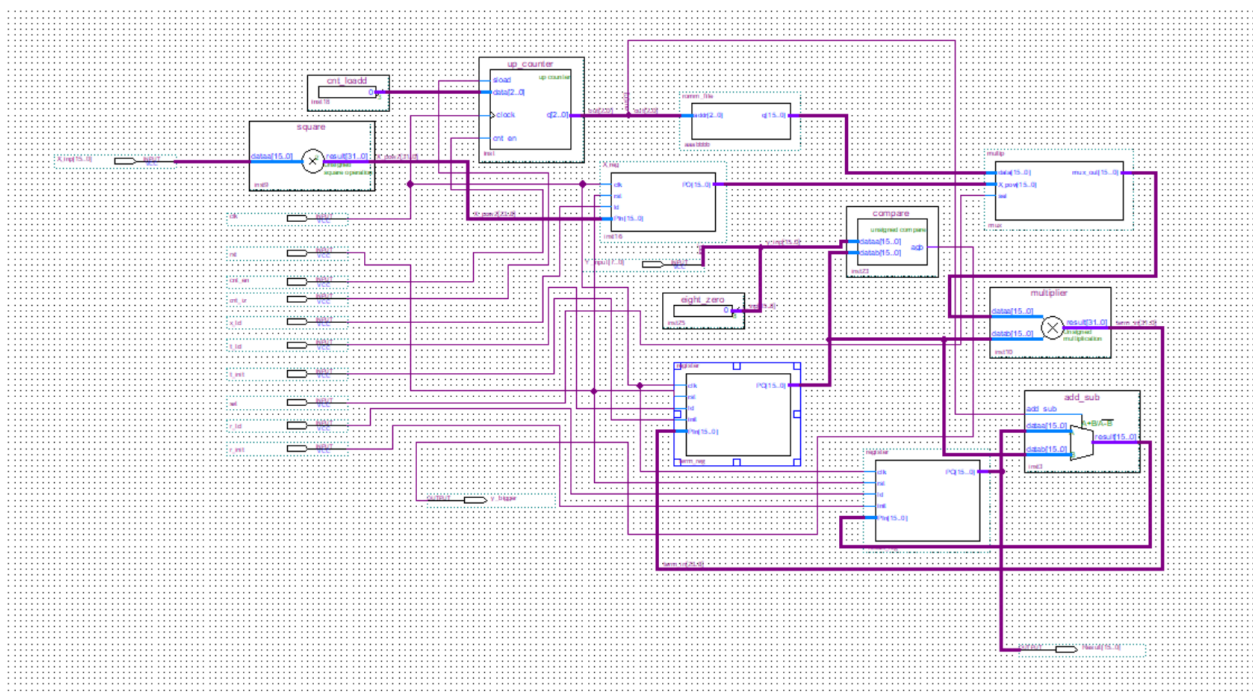

 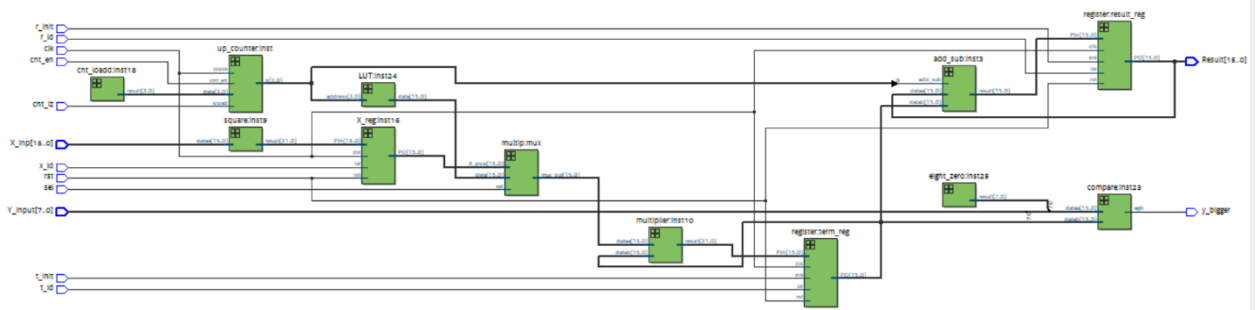



Number of used elements for building datapath:

Flow Status	Successful - Mon Jan 08 18:51:16 2024
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	cos_circuit
Top-level Entity Name	cos_circuit
Family	Cyclone IV GX
Device	EP4CGX15BF14A7
Timing Models	Final
Total logic elements	593 / 14,400 ( 4 % )
Total registers	52
Total pins	51 / 81 ( 63 % )
Total virtual pins	0
Total memory bits	0 / 552,960 ( 0 % )
Embedded Multiplier 9-bit elements	0
Total GXB Receiver Channel PCS	0 / 2 ( 0 % )
Total GXB Receiver Channel PMA	0 / 2 ( 0 % )
Total GXB Transmitter Channel PCS	0 / 2 ( 0 % )
Total GXB Transmitter Channel PMA	0 / 2 ( 0 % )
Total PLLs	0 / 3 ( 0 % )

```
1 module X_reg(input clk,rst,ld,input[15:0] PIn, output reg [15:0] PO);
2     always @(posedge clk,posedge rst) begin
3         if(rst)
4             PO <= 16'b0;
5         else
6             PO <= (ld) ? PIn : PO;
7     end
8 endmodule
```

```
1 module register(input clk,rst,ld,init,input[15:0] PIn, output reg [15:0] PO);
2     always @(posedge clk,posedge rst) begin
3         if(rst)
4             PO <= 16'b0;
5         else if(init)
6             PO <= 16'b0000000011111111;
7         else
8             PO <= (ld) ? PIn : PO;
9     end
10 endmodule
```

### Look Up Table (LUT) Verilog code:

```


1 module romm_file(
2     addr,
3     q
4 );
5 //-----Input Ports-----
6 input [2:0] addr;
7 output reg [15:0] q;
8
9 (* romstyle = "M9K" *) (* ram_init_file = "romm_file.mif" *) reg [15:0] rom [2:0];
10
11     always @ (addr)
12     begin
13         q <= rom[addr];
14     end
15
16 endmodule



```

Addr	+0	+1	+2	+3	+4	+5	+6	+7	ASCII
0	0080	0015	0008	0004	0002	0001	0001	0001	.....

## Final part:

Block diagram:

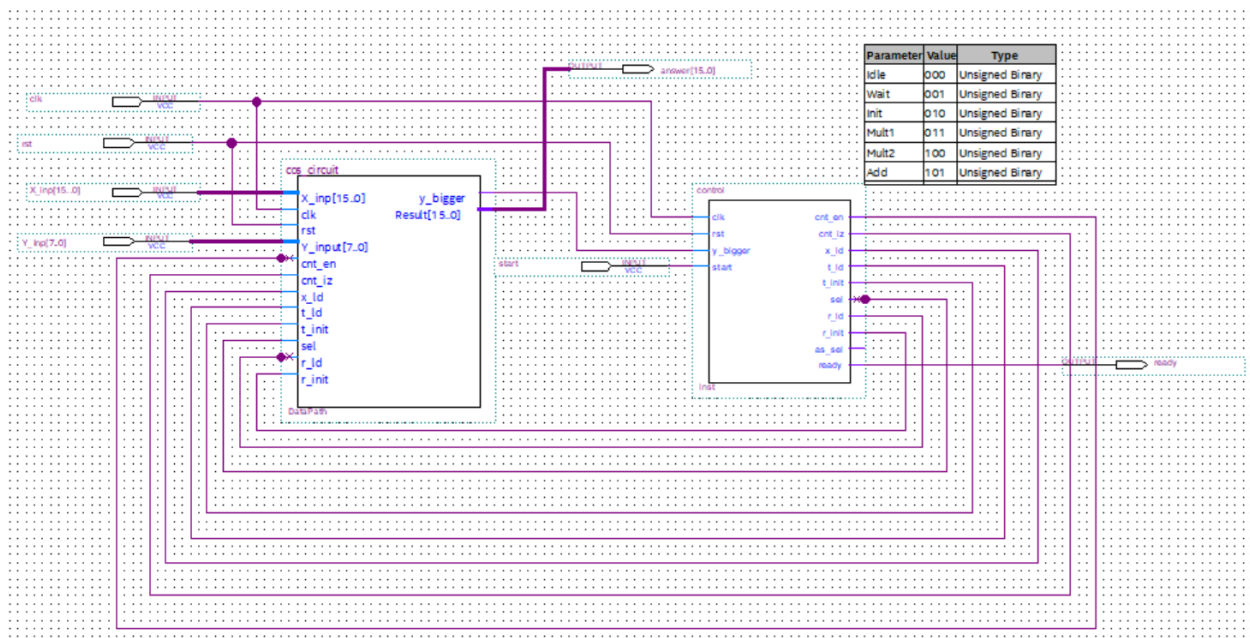

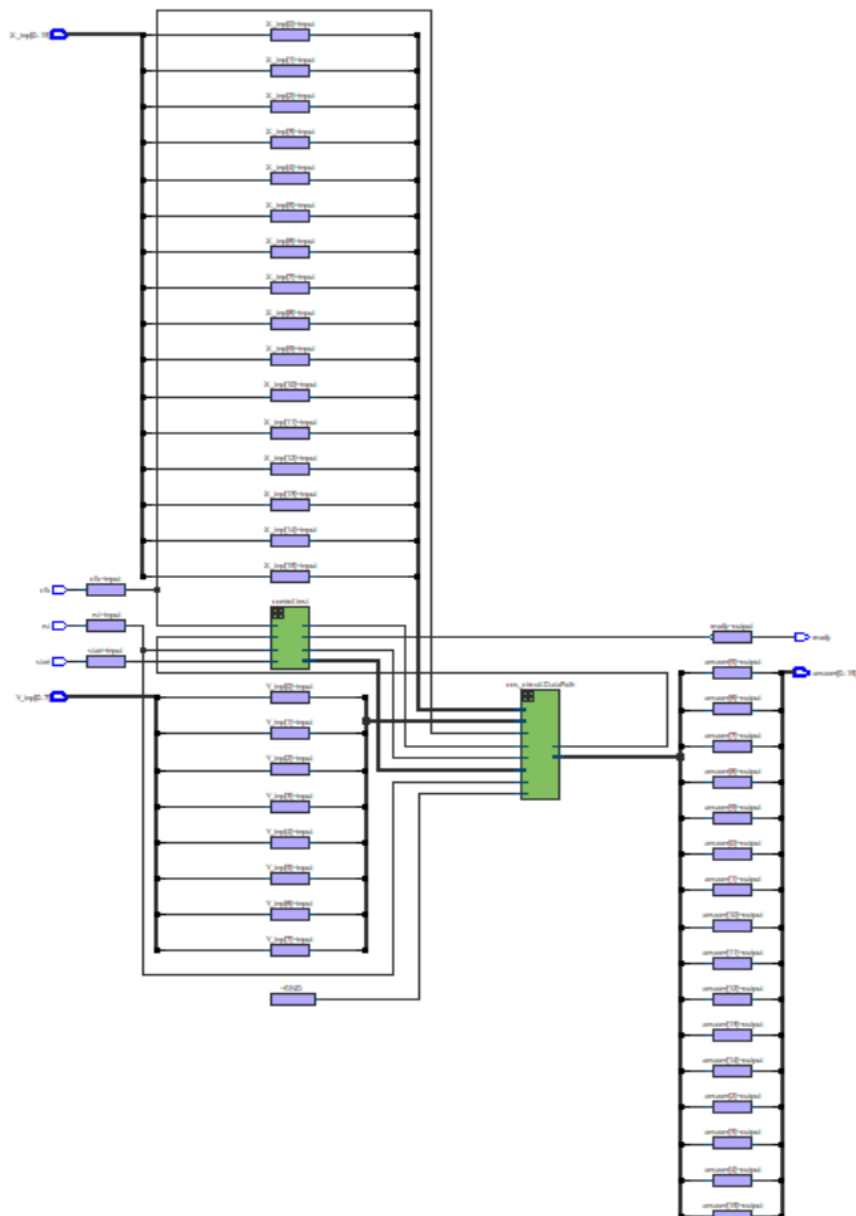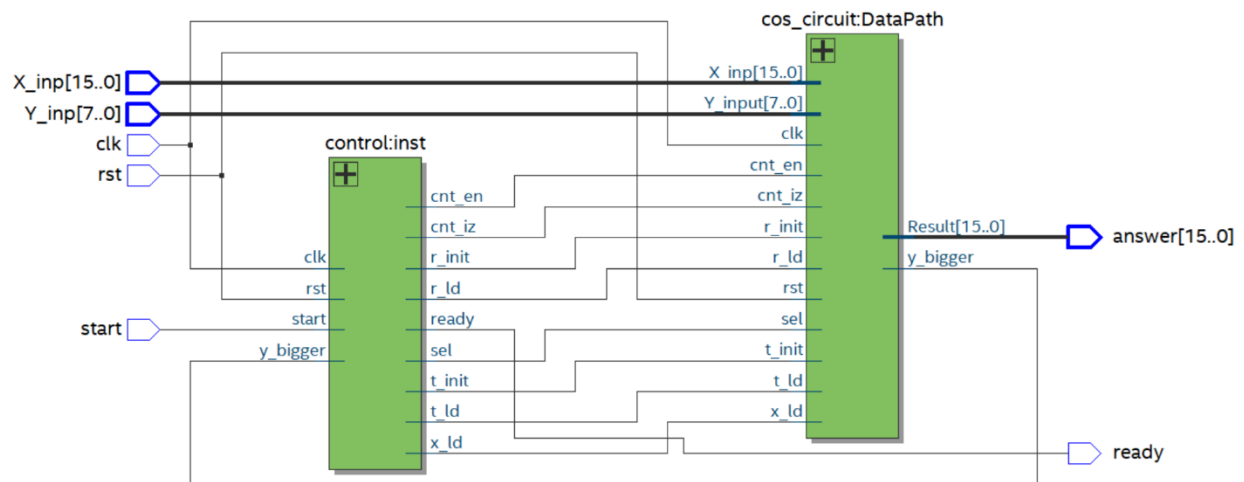


Number of used elements for building the whole circuit:

Flow Status	Successful - Mon Jan 08 19:13:24 2024
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	cosx
Top-level Entity Name	cosx
Family	Cyclone IV GX
Device	EP4CGX15BF14A7
Timing Models	Final
Total logic elements	593 / 14,400 ( 4 % )
Total registers	58
Total pins	44 / 81 ( 54 % )
Total virtual pins	0
Total memory bits	0 / 552,960 ( 0 % )
Embedded Multiplier 9-bit elements	0
Total GXB Receiver Channel PCS	0 / 2 ( 0 % )
Total GXB Receiver Channel PMA	0 / 2 ( 0 % )
Total GXB Transmitter Channel PCS	0 / 2 ( 0 % )
Total GXB Transmitter Channel PMA	0 / 2 ( 0 % )
Total PLLs	0 / 3 ( 0 % )

Testbench and waveform:

```
1 `timescale 1ns/1ns
2 module cosx_tb();
3     reg Start=0,clk=0,rst=0;
4     reg [7:0] y=8'b11111111;
5     reg [15:0] x=16'b0000000110000000;//cos(1.5) -> exact answer: 0.0707 -> my answer: 0.082 (21/255 = 0.082)
6     wire [15:0] Result;
7     wire ready;
8     cos_circuit UUT(ready,clk,rst,y,x,Start,Result);
9     always begin #41;clk=~clk;end
10    initial begin
11        #82;
12        #82;
13        #82;
14        #20; Start = 1;
15        #82; Start=0;
16        #1640;
17        #82;
18        #82;
19        #1640;
20        #82;
21        #82;
22        #82;#82; y=8'b00000001; x=16'b000000011100010;//cos(1.882) -> exact answer: -0.306 -> my answer: -0.301 (The precision has increased with decreasing y)(-77/255 = -0.301)
23        #82; Start = 1;
24        #82; Start=0;
25        #1640;
26        #82;
27        #82;
28        #82;
29        #82;
30        $stop;
31    end
32 endmodule
```

 

Chip planner:

