 


CA3 Report


NOTE: Testbench code and waveform results for all 4 parts is provided in below 2 pictures:

```
testbench.sv
1  `timescale 1ns/1ns
2  module TB();
3      wire signed [15:0] ex1,ex2,yosys1,yosys2;
4      wire zer, neg;
5      logic signed [15:0] inA, inB;
6      logic inC;
7      logic [2:0] opc;
8      ALU_ex1 tb1(ex1,neg,zer,inA,inB,inC,opc);
9      ALU_yosys1 tb2(yosys1,neg,zer,inA,inB,inC,opc);
10     ALU_ex21 tb3(ex2,neg,zer,inA,inB,inC,opc);
11     ALU_yosys2 tb4(yosys2,neg,zer,inA,inB,inC,opc);
12
13     initial begin
14         opc = 3'b000;
15         inC = 1'b1;
16         inA = 16'd243;
17         inB = 16'd3210;
18         inC = 1'b0;
19
20         #200 opc = 3'b000;
21         #200 opc = 3'b001;
22         #200 opc = 3'b010;
23         #200 opc = 3'b011;
24         #200 opc = 3'b100;
25         #200 opc = 3'b101;
26         #200 opc = 3'b110;
27         #200 opc = 3'b111;
28
29         repeat(100000) begin
30             #200
31             inB = $random;
32             opc = $random;
33             inA = $random;
34             inC = $random;
35         end
36         #200 $stop;
37     end
38
39 endmodule
```



 Question 1:

The handwritten hardware of this question is shown below:



Part a: The testbench and results are shown above.

Part b:

Result using yosys library:

```
=== ALU_ex1 ===  
  
Number of wires:          436  
Number of wire bits:      483  
Number of public wires:   7  
Number of public wire bits: 54  
Number of memories:       0  
Number of memory bits:    0  
Number of processes:      0  
Number of cells:          446  
  $_AND_                   63  
  $_AOI3_                   48  
  $_AOI4_                    4  
  $_MUX_                    16  
  $_NAND_                   34  
  $_NOR_                    62  
  $_NOT_                    56  
  $_OAI3_                   43  
  $_OAI4_                   14  
  $_OR_                     15  
  $_XNOR_                   72  
  $_XOR_                    19
```

Result using provided library:

```
5.1.2. Re-integrating ABC results.  
ABC RESULTS:          NAND cells:      183  
ABC RESULTS:          NOR cells:       436  
ABC RESULTS:          NOT cells:       138  
ABC RESULTS:      internal signals:     429  
ABC RESULTS:          input signals:     36  
ABC RESULTS:          output signals:    17
```

Number of cells: 757

Part c: The results are shown in the first page.

Part d: Since part a is made by Verilog using software components such as always and case statement, we don't know what hardware implementation does Verilog use for the statements, in contrast to part c that we yosys simulates the hardware using gates. Also because of considering delays in part c, the waveform of it have x outputs(unlike part a). For evaluating time, it is obvious that part c is slower because it is completely built by hardware and gates. However, we can calculate the times using command "time {run -all} in modelsim like below:

Time for part a:

```
# Break in Module TB at C:/Users/Amin/Documents/Digital-Systems/CA2/testbench.v line 36  
# 370998 microseconds per iteration
```

Time for part c:


```
# Break in Module TB at C:/Users/Amin/Documents/Digital-Systems/CA2/testbench.v line 36  
# 4257442 microseconds per iteration
```

The code of part a:

```
ex1.sv
1  `timescale 1ns/1ns
2  module ALU_ex1(
3      output logic signed [15:0] outW,
4      output neg, zer,
5      input signed [15:0] inA, inB,
6      input inC,
7      input [2:0] opc
8  );
9      always @(inA,inB,inC,opc) begin
10         outW = 16'b0;
11         case(opc)
12             3'b000: outW = ~inA + 1;
13             3'b001: outW = inA + 1;
14             3'b010: outW = inA + inB + inC;
15             3'b011: outW = inA + (inB >>> 1);
16             3'b100: outW = inA & inB;
17             3'b101: outW = inA | inB;
18             3'b110: outW = {inA[7:0], inB[7:0]};
19             3'b111: outW = 16'b0;
20             default : outW = 16'bx;
21         endcase
22     end
23     assign neg = outW[15];
24     assign zer = ~|outW;
25 endmodule
```

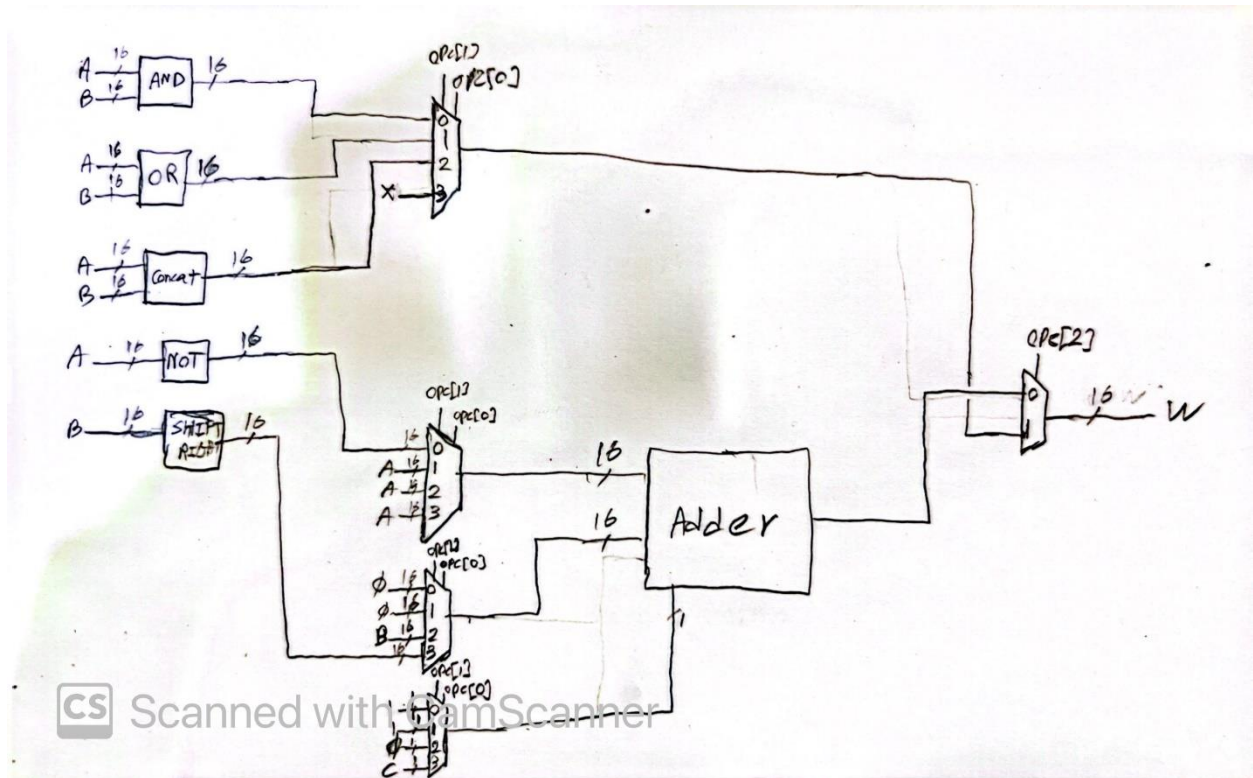Question 2:

The handwritten hardware of this question is shown below:



Part a: The testbench and results are shown in the first page.

Part b:

Result using yosys library (next page):

```
=== design hierarchy ===
```

ALU_ex2	1
AB_AND	1
AB_CONCAT	1
AB_OR	1
COMPLEMENT	1
FIRST40PS	1
LAST30PS	1
MUX4TO1A	1
MUX4TO1B	1
MUX4TO1CONTROL	1
SHIFT	1

Number of wires:	213
Number of wire bits:	793
Number of public wires:	50
Number of public wire bits:	630
Number of memories:	0
Number of memory bits:	0
Number of processes:	0
Number of cells:	293
\$_AND_	30
\$_AOI3_	11
\$_MUX_	80
\$_NAND_	19
\$_NOR_	23
\$_NOT_	56
\$_OAI3_	9
\$_OR_	32
\$_XNOR_	16
\$_XOR_	17

As we can see, the number is so much decreased (from 446 to 293).

Result using provided library (for all modules in my code):

4.1.2. Re-integrating ABC results.

ABC RESULTS:	NOR cells:	16
ABC RESULTS:	NOT cells:	32
ABC RESULTS:	internal signals:	0
ABC RESULTS:	input signals:	32
ABC RESULTS:	output signals:	16

Removing temp directory.

AB_AND

4.3.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	16
ABC RESULTS:	NOT cells:	32
ABC RESULTS:	internal signals:	0
ABC RESULTS:	input signals:	32
ABC RESULTS:	output signals:	16

Removing temp directory.

AB_OR

4.5.2. Re-integrating ABC results.

ABC RESULTS:	NOT cells:	16
ABC RESULTS:	internal signals:	0
ABC RESULTS:	input signals:	16
ABC RESULTS:	output signals:	16

COMPLEMENT

4.6.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	37
ABC RESULTS:	NOR cells:	110
ABC RESULTS:	NOT cells:	48
ABC RESULTS:	internal signals:	75
ABC RESULTS:	input signals:	33
ABC RESULTS:	output signals:	16

FIRST4OPS

4.7.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	34
ABC RESULTS:	NOR cells:	50
ABC RESULTS:	NOT cells:	34
ABC RESULTS:	internal signals:	19
ABC RESULTS:	input signals:	50
ABC RESULTS:	output signals:	16

LAST3OPS

4.8.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	1
ABC RESULTS:	NOR cells:	49
ABC RESULTS:	NOT cells:	2
ABC RESULTS:	internal signals:	1
ABC RESULTS:	input signals:	34
ABC RESULTS:	output signals:	16

MUX4TO1A

4.9.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	32
ABC RESULTS:	NOR cells:	32
ABC RESULTS:	NOT cells:	16
ABC RESULTS:	internal signals:	53
ABC RESULTS:	input signals:	34
ABC RESULTS:	output signals:	16

MUX4TO1B

4.10.2. Re-integrating ABC results.

ABC RESULTS:	NAND cells:	2
ABC RESULTS:	NOT cells:	1
ABC RESULTS:	internal signals:	1
ABC RESULTS:	input signals:	3
ABC RESULTS:	output signals:	1

MUX4TO1CON

AB_CONCAT

Extracted 0 gates and 0 wires to a netlist network with 0 inputs and 0 outputs.

SHIFT

```
Extracted 0 gates and 0 wires to a netlist network with 0 inputs and 0 outputs.
```

ALU_ex2(main module):

```
4.4.2. Re-integrating ABC results.  
ABC RESULTS:          NAND cells:      58  
ABC RESULTS:          NOR cells:       5  
ABC RESULTS:          NOT cells:      49  
ABC RESULTS:      internal signals:    14  
ABC RESULTS:      input signals:      33  
ABC RESULTS:      output signals:     17
```

Number of cells: 672

Part c: The results are shown in the first page.

Part d: Like question 1, since part a is made by Verilog using software components such as always and case statement, we don't know what hardware implementation does Verilog use for the statements, in contrast to part c that we yosys simulates the hardware using gates. Also because of considering delays in part c, the waveform of it have x outputs(unlike part a). For evaluating time, it is obvious that part c is slower because it is completely built by hardware and gates.

However, we can calculate the times using command “time {run -all} in modelsim like below:

Time for part a:

```
# Break in Module TB at C:/Users/Amin/Documents/Digital-Systems/CA2/testbench.v line 36
# 3546125 microseconds per iteration
```

Time for part c:

```
# Break in Module TB at C:/Users/Amin/Documents/Digital-Systems/CA2/testbench.v line 36
# 4126897 microseconds per iteration
```

Code of part a is show below:

```
1 timescale 1ns/1ns
2 module AB_AND1(output signed [15:0]out,input signed [15:0] inA,input signed [15:0] inB);
3     assign out = inA & inB;
4 endmodule
5
6 module AB_OR1(output signed [15:0]out,input signed [15:0] inA,input signed [15:0] inB);
7     assign out = inA | inB;
8 endmodule
9
10 module AB_CONCAT1(output signed [15:0]out,input signed [15:0] inA,input signed [15:0] inB);
11     assign out = {inA[7:0], inB[7:0]};
12 endmodule
13
14 module COMPLEMENT1(output signed [15:0]out,input signed [15:0] inA);
15     assign out = ~inA;
16 endmodule
17
18 module SHIFT1(output signed [15:0]out,input signed [15:0] inB);
19     assign out = inB >>> 1;
20 endmodule
21
22
23 module MUX4TO1A1(output signed [15:0]out,input [2:0] opc,input signed [15:0] inA,input signed [15:0] inA_comp);
24     assign out =
25         (opc[1:0] == 2'b00) ? inA_comp:
26         ((opc[1:0] == 2'b01) || (opc[1:0] == 2'b10) || (opc[1:0] == 2'b11)) ? inA:
27         16'bx;
28 endmodule
29
30 module MUX4TO1B1(output signed [15:0]out,input [2:0] opc,input signed [15:0] inB,input signed [15:0] inB_shifted);
31     assign out =
32         ((opc[1:0] == 2'b00) || (opc[1:0] == 2'b01)) ? 16'b0:
33         (opc[1:0] == 2'b10) ? inB:
34         (opc[1:0] == 2'b11) ? inB_shifted:
35         16'bx;
36 endmodule
37
38 module MUX4TO1CONTROL1(output out,input [2:0] opc,input inC);
39     assign out =
40         ((opc[1:0] == 2'b00) || (opc[1:0] == 2'b01)) ? 1'b1:
41         (opc[1:0] == 2'b10) ? inC:
42         (opc[1:0] == 2'b11) ? 1'b0;
```

```

44 | 16'b0;
45 | endmodule
46 | module FIRST4OPS1(output signed [15:0] out,input signed [15:0] inA_new,input signed [15:0] inB_new,input inC_new);
47 |     assign out = inA_new + inB_new + inC_new;
48 | endmodule
49 |
50 | module LAST3OPS1(output signed [15:0] out,input [2:0] opc,input signed [15:0] A_B_anded,input signed [15:0] A_B_concat,input signed [15:0] A_B_ored);
51 |     assign out =
52 |         (opc[1:0] == 2'b00) ? A_B_anded:
53 |         (opc[1:0] == 2'b01) ? A_B_ored:
54 |         (opc[1:0] == 2'b10) ? A_B_concat:
55 |         16'b0;
56 | endmodule
57 |
58 |
59 | module ALU_ex21(
60 |     output logic signed [15:0] outW,
61 |     output neg, zer,
62 |     input signed [15:0] inA, inB,
63 |     input inC,
64 |     input [2:0] opc
65 | );
66 |     wire control_mux;
67 |     wire[15:0] a_mux, b_mux, a_comp, b_shift, a_b_ored, a_b_anded, a_b_concat, first4ops, last3ops;
68 |     AB_AND anding(a_b_anded,inA,inB);
69 |     AB_OR oring(a_b_ored,inA,inB);
70 |     AB_CONCAT concating(a_b_concat,inA,inB);
71 |     COMPLEMENT complementing(a_comp,inA);
72 |     SHIFT shifting(b_shift,inB);
73 |     MUX4TO1A A_mux(a_mux,opc,inA,a_comp);
74 |     MUX4TO1B B_mux(b_mux,opc,inB,b_shift);
75 |     MUX4TO1CONTROL Control_mux(control_mux,opc,inC);
76 |     FIRST4OPS F_OPS(first4ops,a_mux,b_mux,control_mux);
77 |     LAST3OPS L_OPS(last3ops,opc,a_b_anded,a_b_concat,a_b_ored);
78 |     assign outW =
79 |         (opc[2] == 2'b0) ? first4ops:
80 |         (opc[2] == 2'b1) ? last3ops:
81 |         16'b0;
82 |     assign neg = outW[15];
83 |     assign zer = ~|outW;
84 | endmodule

```

Question 3: If we compare the synthesis results in question 1 and 2, we can find out that question 2 ALU is much more efficient because of the hardware implementation and using a little creative and tricky way for optimizing that is sharing the hardware and minimizing it as much as we can. But this way is much harder to design and a bit slower.