 


CA4 Report

Question1:

Part a , b:



Code:


```

1  `timescale 1ns/1ns
2  module sr_latch_2inp (input S, R, output Q, Qb);
3      nand #8 Snand (Q, Qb, S);
4      nand #8 Rnand (Qb, Q, R);
5  endmodule
6
7  module sr_latch_3inp (input S1, R1, S2, R2, output Q, Qb);
8      nand #12 Snand (Q, S1, S2, Qb);
9      nand #12 Rnand (Qb, R1, R2, Q);
10 endmodule

```

Test bench:


```
1  `timescale 1ns/1ns
2  module q1_tb ();
3      logic S,R;
4      wire Q1, QB1;
5      wire Q2, QB2;
6      sr_latch_2inp _2inp(S, R, Q1, QB1);
7      sr_latch_3inp _3inp(S, R, S, R, Q2, QB2);
8
9      initial begin
10         S = 0; R = 1;
11         #200 S = 0; R = 1;
12         #200 S = 1; R = 1;
13         #200 S = 1; R = 0;
14         #200 S = 0; R = 0;
15         #200 S = 1; R = 0;
16         #200 S = 0; R = 0;
17         #200 S = 1; R = 1;
18         #200 S = 1; R = 0;
19         #100 $stop;
20     end
21
22 endmodule
```

 

Part c:

If S and R are simultaneously active (00 in this case because they are active low), there will be memory loss. For example if the input after 00 is 11, the output must be Q but because of the loss of memory, the output is unknown (goes into a loop of 0 and 1's)

Question 2:

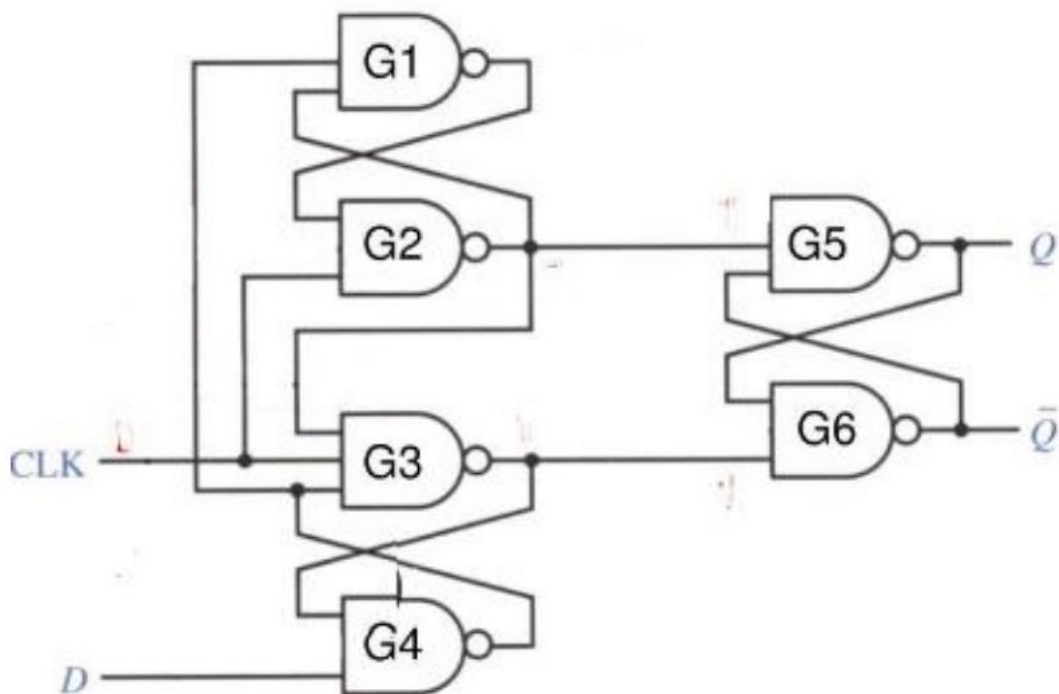

Part a:

Code:


```
1  `timescale 1ns/1ns
2  module Edge_DFF (input D , clk, output Q, Qb);
3      wire G1_o,G2_o,G3_o,G4_o;
4      sr_latch_2inp G1_G2(G4_o,clk,G1_o,G2_o);
5      sr_latch_3inp G3_G4(G2_o,D,clk,D,G3_o,G4_o);
6      sr_latch_2inp G5_G6(G2_o,G3_o,Q,Qb);
7  endmodule
```

Testbench:

```
1  `timescale 1ns/1ns
2  module q2_tb();
3      logic d = 1, clk = 0;
4      wire Q, Qb;
5      Edge_DFF DFF (d, clk, Q, Qb);
6      always #100 clk = ~clk;
7      initial begin
8          repeat (20) #150 d = $random;
9          #200 $stop;
10     end
11 endmodule
```

Part b:

Testbench:

 


At the positive edge of clock, the output Q becomes the d value.

When d changes from 1 to 0, the delay for changing Q and Qb are:

Q : 28ns


Qb: 20ns

 

When d changes from 0 to 1, the delay for changing Q and Qb are:

Q : 16ns

Qb: 24ns

 


Part c:

$T_{\text{setup}} = (12 + \epsilon)\text{ns} \rightarrow 13\text{ns}$

Testbench for calculating T_{setup} :

```
1  `timescale 1ns/1ns
2  module q2_tb();
3      logic d = 0, clk = 0;
4      wire Q, Qb;
5      Edge_DFF DFF (d, clk, Q, Qb);
6      always #100 clk = ~clk;
7      initial begin
8          #50 d = 1;
9          #238 d = 0;
10         #300 $stop;
11     end
12 endmodule
```

Waveform for calculating T_{setup} :

 


Part d:

Thold = $(0 + \epsilon)\text{ns} \rightarrow 1\text{ns}$


Testbench for calculating Thold:

```
1  `timescale 1ns/1ns
2  module q2_tb();
3      logic d = 1, clk = 0;
4      wire Q, Qb;
5      Edge_DFF DFF (d, clk, Q, Qb);
6      always #200 clk = ~clk;
7      initial begin
8          #50 d = 0;
9          #200 d = 1;
10         #50 d = 0;
11         #300 $stop;
12     end
13 endmodule
```

Waveform for calculating Thold:

 

Question 3:

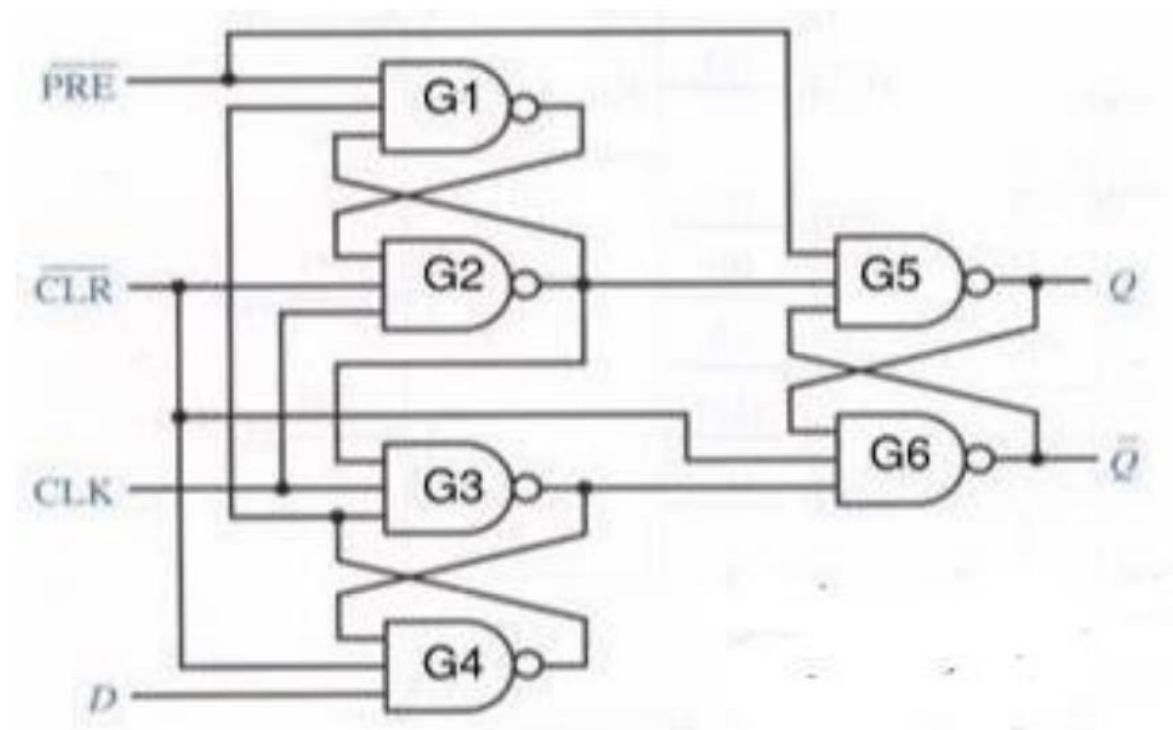

Part e:

```
1  `timescale 1ns/1ns
2  module PC_DFF (input D , clk, PRE, CLR, output Q, Qb);
3      wire G1_o,G2_o,G3_o,G4_o;
4      sr_latch_3inp G1_G2(PRE,CLR,G4_o,clk,G1_o,G2_o);
5      sr_latch_3inp G3_G4(G2_o,CLR,clk,D,G3_o,G4_o);
6      sr_latch_3inp G5_G6(PRE,CLR,G2_o,G3_o,Q,Qb);
7  endmodule
```


Testbench:

```
1  `timescale 1ns/1ns
2  module q3_tb();
3      logic d = 0, clk = 0, pre = 1, clr = 1;
4      wire Q, Qb;
5      PC_DFF pcdff (d, clk, pre, clr, Q, Qb);
6      always #100 clk = ~clk;
7      initial begin
8          repeat (20) #150 {d,pre,clr} = $random;
9          #200 $stop;
10     end
11 endmodule
```


Part f:

change D from 0 to 1: Q = 24ns and Qb = 36ns

change D from 1 to 0: Q = 36ns and Qb = 24ns

PRE active: Q = 12ns and Qb = 48ns

CLR active: Q = 24ns and Qb = 12ns

 

Part g:

Nothing happens if clock activates while preset or clear are already active because preset and clear are asynchronous in this flip flop and they have priority to clock.

Part h:

Active Preset: $Q = 1$

Active CLR : $Q = 0$

Active CLR and Preset simultaneously: Memory loss($Q = Q_b$)